

Circuit Analysis (Lab10)

Experiment 9: Verification of Thevenin's Theorem

Name: Registration No:

Date: Grade and Signature:

CLO2 CLO3	Use with identification the circuit components, breadboards, multimeter, power supplies, signal generators, and oscilloscopes. Make measurements in their own constructed electric circuits.			
Psychomotor/Affective	Level1 (1)	Level2 (2-3)	Level3 (4-5)	Level4 (6-7)
Report Marks (3)				
	Total marks (10)			

Objective

The objective of this lab is verify Thevenin's theorem and to find the full load current.

Apparatus Required

Sr. no	Apparatus	Range	Quantity
1	Regulated Power Supply	Standard	1
2	Signal Generator	Standard	1
3	Oscilloscope	Standard	1
4	Digital Multimeter	Standard	1
5	Breadboard & Wires	Standard	As Required
6	Resistors	1k, 330 ohms	1,3
7	Potentiometer	Standard	1

Description

Statement:



Any linear bilateral, active two terminal network can be replaced by an equivalent voltage source (VTH). Thevenin's voltage or V_{OC} in series with looking back resistance R_{TH} .

Precautions:


1. Voltage control knob of RPS should be kept at minimum position.
2. Current control knob of RPS should be kept at maximum position

Procedure:


1. Connections are given as per the circuit diagram.
2. Set a particular value of voltage using RPS and note down the corresponding ammeter readings. To find V_{TH}
3. Remove the load resistance and measure the open circuit voltage using multimeter (V_{TH}). To find R_{TH}
4. To find the Thevenin's resistance, remove the RPS and short circuit it and find the R_{TH} using multimeter.
5. Give the connections for equivalent circuit and set V_{TH} and R_{TH} and note the corresponding ammeter reading.
6. Verify Thevenin's theorem.

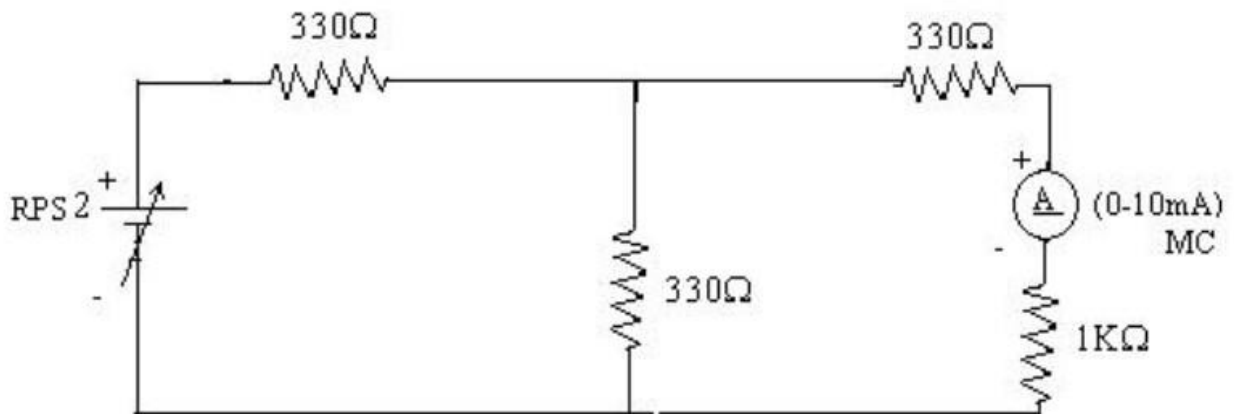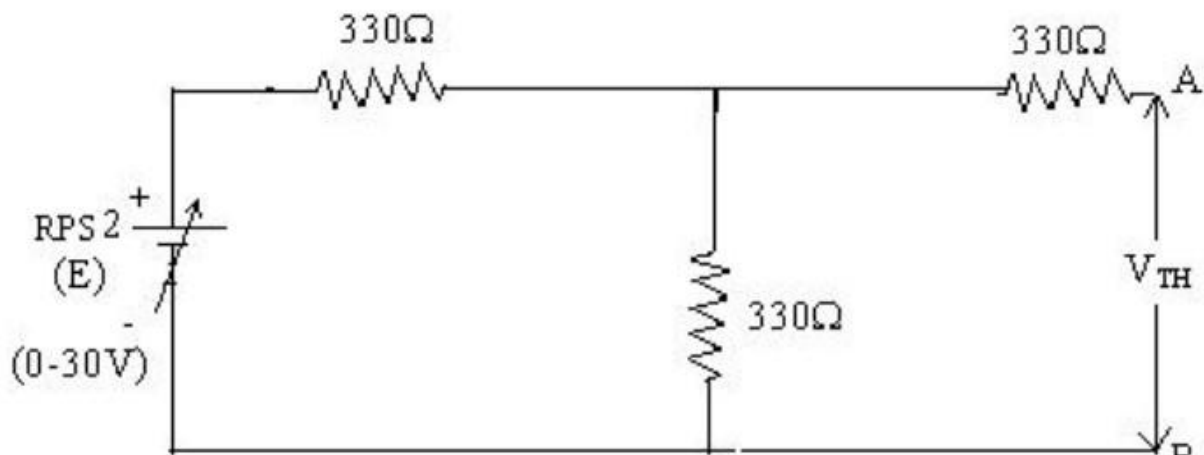Circuit - 1: To find load current**To find V_{TH}** 

To find R_{TH}

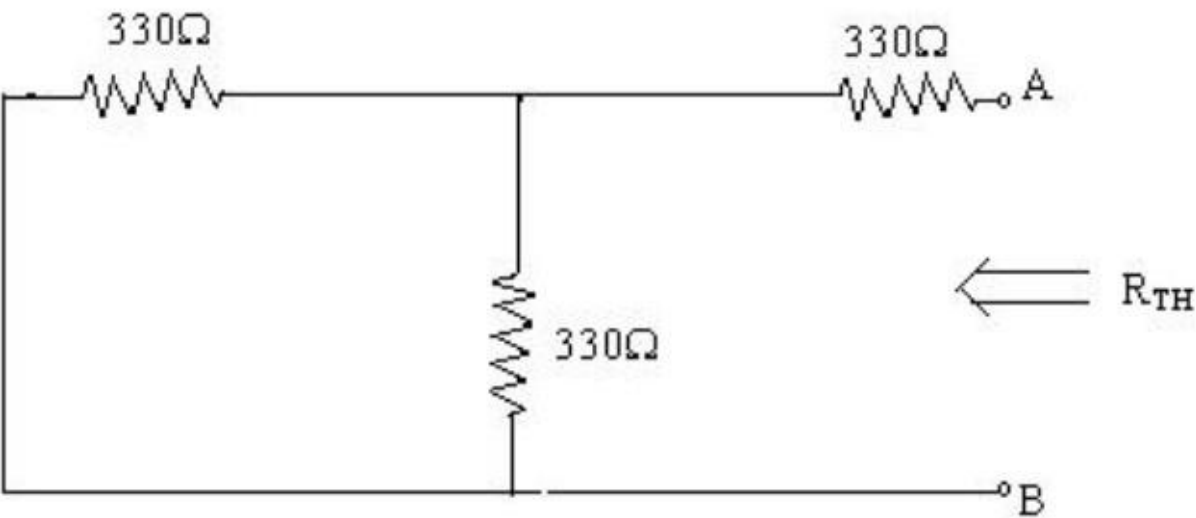

Thevenin's Equivalent circuit:

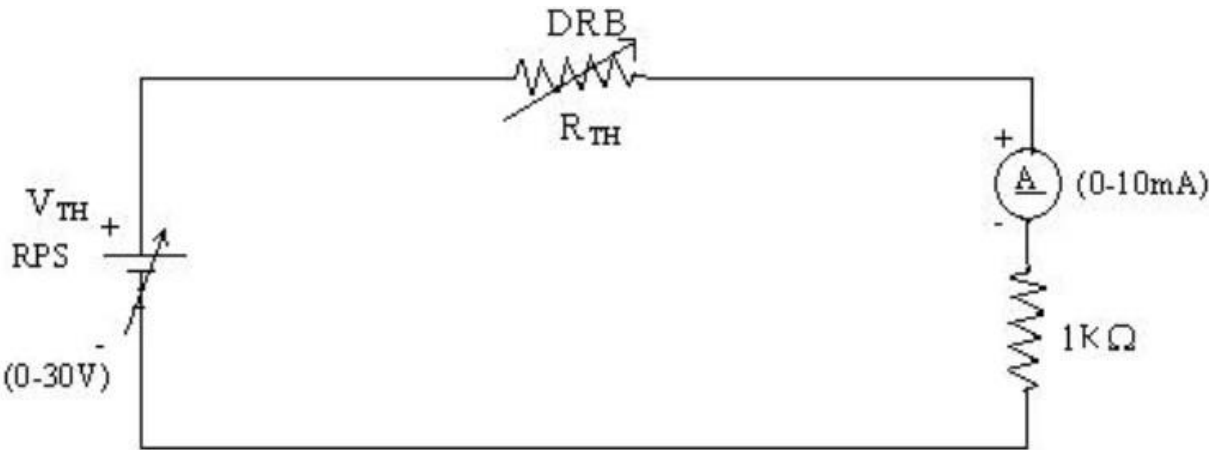

Thevenin Practical Values

	E(V)	$V_{TH}(V)$	$R_{TH}(ohms)$	I_L (mA)	
				Circuit - I	Equivalent Circuit
Values					

Post Lab Questions

1. What is Thevenin's Theorem?

2. What are the applications of Thevenin's Theorem?

3. What are the theoretical and practical limitations of Thevenin's Theorem?
